

2021

Full Marks : 70

Time : 3 hours

Answer from all the Sections as directed.

Candidates are required to give their answers in their own words as far as practicable.

## SECTION—A

( Compulsory )

Objective questions of 2 marks each.

1. Choose the correct answer from the following :

(a) The current gain in the common base configuration is less than 1 because

(i)  $I_e < I_b$

(ii)  $I_e < I_c$

(iii)  $I_b < I_e$

(iv)  $I_c < I_e$

(b) Least doped region in a transistor is

(i) Either emitter or collector

(ii) Base

(iii) Emitter

(iv) Collector

(c) In a p-n-p transistor the base is the n-region. Its width relative to the p-region is

(i) Smaller

(ii) Larger

(iii) Same

(iv) Not related

(d) For a transistor amplifier the power gain and voltage gain are 7.5 and 2.5 respectively. The value of current gain will be

(i) 0.33

(ii) 0.66

(iii) 0.99

(iv) 3

( Turn Over )

UDHB-Sem-IV-Phy(CC-10)

( Continued )

( 3 )

- (c) With zero volt on both the input, the Op-Amp ideally should have an output
- (i) Equal to positive supply voltage
  - (ii) Equal to negative supply voltage
  - (iii) Zero
  - (iv) Equal to CMMR
- (f) For an Op-Amp with negative feedback, the output is
- (i) Equal to the input
  - (ii) Increased
  - (iii) Fed back to the inverting input
  - (iv) Fed back to the non-inverting input
- (g) A voltage follower ———.
- (i) Has voltage gain of 1
  - (ii) Non inverting
  - (iii) Has no feedback resistor
  - (iv) Has all of these

( 4 )

- (h) An oscillator produces ——— oscillations.
- (i) Damped
  - (ii) Undamped
  - (iii) Modulated
  - (iv) None of the above
- (i) Hartley oscillator is commonly used in
- (i) Radio receiver
  - (ii) Radio transmitter
  - (iii) TV receiver
  - (iv) None of these
- (j) \_\_\_\_\_ is fixed frequency oscillator
- (i) Phase shift oscillator
  - (ii) Hartley oscillator
  - (iii) Colpitt's oscillator
  - (iv) Crystal oscillator

## SECTION--II

Short answer type questions of 5 marks each,  
any *four* to be answered :

2. Discuss the principle of phase shift oscillator.
3. Define the conductivity and mobility of a p-n junction diode.
4. Make a neat circuit diagram for the full wave bridge rectifier circuit and define ripple factor.
5. For a subtractor circuit using Op-Amp, input voltages are  $v_1 = 5V$  and  $v_2 = 2V$  and resistances  $R_1 = 10k$  and  $R_2 = 20k$ , respectively. Calculate the output voltage. <https://www.jharkhandstudy.com>
6. Discuss the frequency response of an Op-Amp.
7. Draw the circuit of a RC coupled amplifier and discuss its frequency response.
8. Write short note on Solar Cell.

9. Discuss in brief the construction and functioning of a photodiode.

## SECTION--III

Long answer type questions of 15 marks each,  
any *two* to be answered :

10. (a) Draw the block diagram of an Op-Amp and explain its detail. Describe the ideal characteristics of it.
  - (b) For a non-inverting amplifier, given that the voltage is  $6V$ ,  $R_1 = 2 k\Omega$  and  $R_f = 10 k\Omega$ , calculate the output voltage.
11. (a) Explain the Colpits oscillator, with neat circuit diagram and derive the expression for frequency of the oscillator with neat circuit diagram.
  - (b) Design and draw a circuit of Colpits oscillator, for obtaining the signal of 10 kHz.
12. (a) Discuss the construction of a p-n junction diode.

- (b) Obtain the I-V relationship for a p-n junction diode. Plot the graph and explain it.
13. (a) Discuss the relationship between  $I_E$ ,  $I_C$  and  $I_B$  for n-p-n transistor.
- (b) Obtain the relation for  $\alpha$  and  $\beta$  for n-p-n transistor. Show it graphically.

---

<https://www.jharkhandstudy.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से